

EGB240 Electronic Design

Assessment 1: PCB Siren Circuit Design Portfolio

Submitted 8/04/2022

Hari Markonda Patnaikuni (n10789511)

Executive Summary

The following portfolio comprises of the design progression of a two-tone PCB Siren Circuit which includes the theoretical, experimental, and simulation processes used to achieve the final PCB design. The design was created to meet following specifications:

- Power by two AA batteries (3V supply)
- Siren to be turned on and off using a slide switch
- First oscillating frequency of 0.296 Hz to alternate between two tones
- First tone frequency of 4.44 kHz
- Second tone frequency of 2.051 kHz
- Total supply current of 0.02A
- The dimensions of the PCB are 54 x 28 (without the battery holder)


The design is built on a double layer PCB.

The design uses two polyester greencap capacitors and one polarised electrolytic capacitor. Also, the design utilises a Piezoelectric buzzer to output the two tones, two 1N4148 diodes, resistors, and a Hex inverting Schmitt trigger.

Contents

1. Circuit schematic	2
2. Summary of design and operation	3
3. PCB layout	5
4. Bill of materials.....	6
5. Assembly overlay	7
6. Photos of assembled prototype	8
7. Simulation circuit and results.....	9
Simulation model netlist (LTspice)	10
Simulation model SW plot (LTspice)	11
Simulation model TONE1 plot (LTspice)	12
Simulation model TONE2 plot (LTspice)	13
Simulation model TONE1 and TONE2 plot (LTspice)	14
Simulation model C2 charge and discharge plot (LTspice)	15
Simulation model C3 charge and discharge plot (LTspice)	16
8. Experimental results	17
References	21

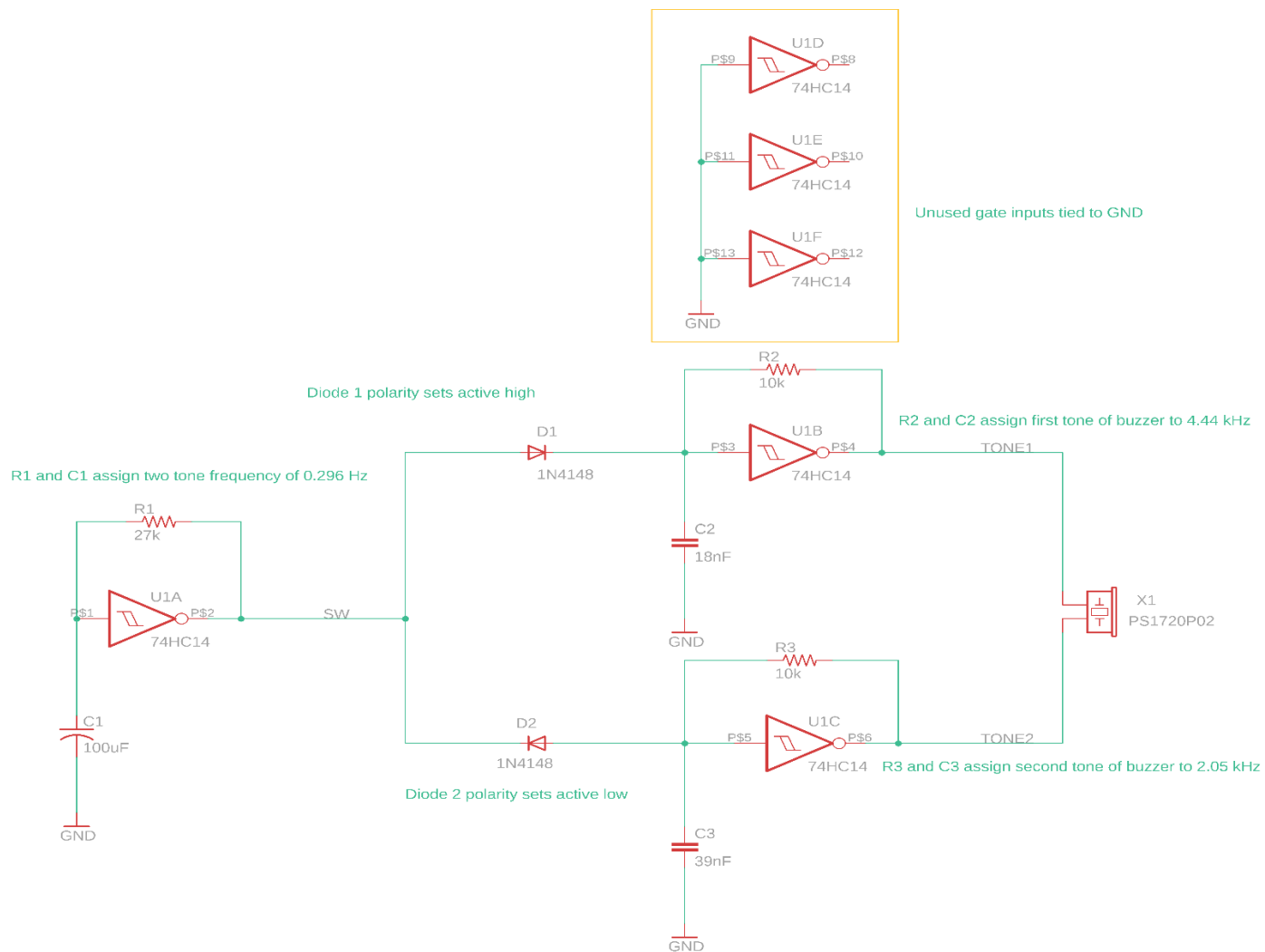R1 and C1 assign two tone frequency of 0.296 Hz



Page 2 of 21

2. Summary of design and operation


To begin with, the design for this siren followed the information given in the datasheets of both the Piezoelectric buzzer and the Hex inverting Schmitt trigger.

The below equation was the key indicator for deciding on component values for the oscillators.

$$f = \frac{1}{T} = \frac{1}{k \times C \times R}$$

The k value shown in the above equations can be determined by referring to Fig 15 K-factor for 74HC14 which is found on page 12 of the 74HC14 Hex inverting Schmitt trigger datasheet. The referenced graph is shown below.

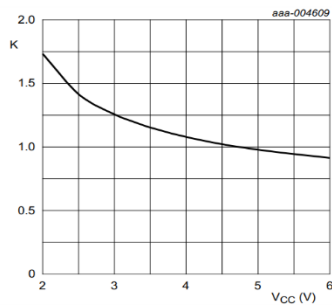In addition to this, the target frequencies of both tones for the siren were determined to be at least 1 kHz and the high tone to be close to the 5 kHz peak in sound pressure as shown in the below Frequency and Sound Pressure Characteristics graph found in the PS1720P02 Piezoelectric buzzer datasheet.



K-factor for 74HC14

Fig 15. Typical K-factor for relaxation oscillator

Figure 2 - K-factor for 74HC14 (NXP, 2012)

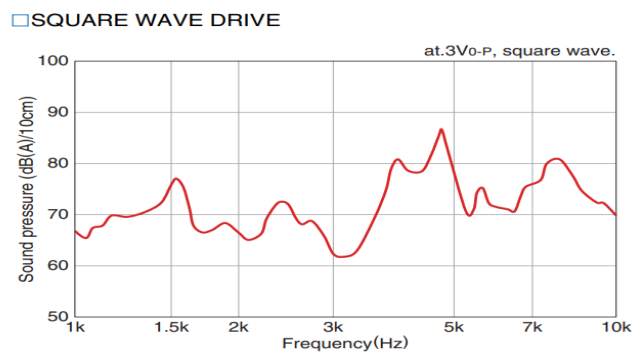


Figure 3 - Frequency and Sound Pressure Characteristics for PS1720P02 Buzzer (TDK, 2022)

As seen in the above graph for a circuit with a 3V VCC the K-factor is equal to 1.25. Hence, the K-factor used to calculate the frequency will be 1.25.

The siren design shown in section 1 of the report has three key segments which are required to achieve a two-tone siren. By utilising three relaxation oscillators this two-tone siren is attained. Three gates of a Schmitt trigger for the three oscillators. The model of the Schmitt trigger is a 74HC14 Hex inverting Schmitt trigger.

The first relaxation oscillator acts as a trigger oscillator due to its small inaudible frequency of 0.296 Hz. Two standard component values of 27kΩ and 100μF for the resistor and capacitor were used to calculate this oscillating frequency. The below calculations theoretically validate this.

$$f = \frac{1}{1.25 \times 100 \times 10^{-6} \times 27k}$$
$$f = 0.296 \text{ Hz}$$

The topmost relaxation oscillator produces a frequency of 4.44 kHz due to the resistor and capacitor values being $10k\Omega$ and $18nF$ respectively. Below are the calculations which verify this frequency value.

$$f = \frac{1}{1.25 \times 18 \times 10^{-9} \times 10k}$$

$$f = 4.44 \text{ kHz}$$

\therefore tone produced is 4.44 kHz.

Whereas the bottom relaxation oscillator produces a frequency of 2.051 kHz due to the resistor and capacitor values being $10k\Omega$ and $39nF$ respectively. The below calculations verify this frequency value.

$$f = \frac{1}{1.25 \times 39 \times 10^{-9} \times 10k}$$

$$f = 2.051 \text{ kHz}$$

\therefore tone produced is 2.051 kHz.

In addition to these components, two 1N4148 diodes were used to enable the altering between the two tones with the first diode being mirrored to the right when compared with the second diode. These diodes were placed just before each of the relaxations oscillators which are producing the audible tones. The buzzer used for this circuit is a PS1720P02 buzzer which is connected to both outputs of the audible oscillators. Finally, the switch used is an SS-12 which is used to turn the circuit on and off.

3. PCB layout

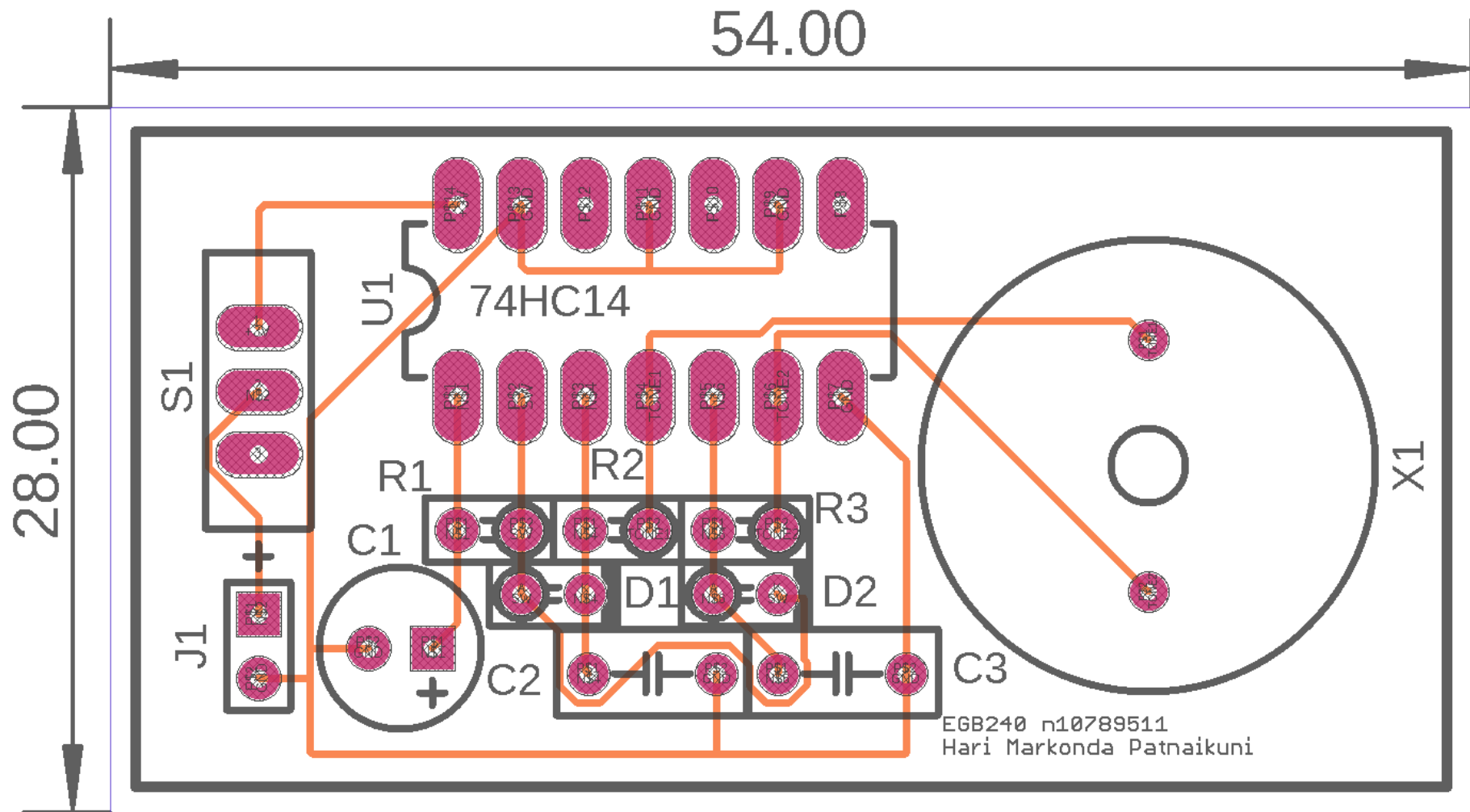



Figure 4 - Siren circuit PCB layout with board dimensions in millimetres.

4. Bill of materials

Designator	Value	Description	Qty	Footprint		
C1	100uF	Capacitor, Polarised, RB, 2.5mm pitch	1	CAP-RB-P2.54-D6.3		
C2	18nF	Capacitor, Polyester/Mylar (Greencap), 5mm pitch	1	CAP-GREEN-7.5X3.2-P5.08		
C3	39nF	Capacitor, Polyester/Mylar (Greencap), 5mm pitch	1	CAP-GREEN-7.5X3.2-P5.08		
D1	1N4148	Diode, Axial, DO-35	1	DO35-P2.54		
D2	1N4148	Diode, Axial, DO-35	1	DO35-P2.54		
J1	2xAA	Battery holder, 3V, 2xAA, flying leads	1	BATT-3V		
R1	27k	Resistor, Axial, 0.25W	1	AXIAL-P2.54		
R2	10k	Resistor, Axial, 0.25W	1	AXIAL-P2.54		
R3	10k	Resistor, Axial, 0.25W	1	AXIAL-P2.54		
S1		Switch, SPDT, Slide, On-On	1	SS-12		
U1	74HC14	Hex schmitt trigger INVERTER	1	DIP-14		
U1		IC socket, DIP-14	1	DIP-14		
X1	PS1720P02	Piezoelectric Buzzer	1	PS1720P02		
Designator	Manufacturer	MPN	Supplier	SKU	MOQ	Price
C1	Generic	Capacitor, Polarised, Electrolytic, 100uF 25V, Radial, 2.5mm pitch	Jaycar	RE6140	1	\$0.45
C2	Generic	Capacitor, Polyester Greencap, 18nF 100V, 5mm pitch	Jaycar	RG5080	1	\$0.30
C3	Generic	Capacitor, Polyester Greencap, 39nF 100V, 5mm pitch	Jaycar	RG5100	1	\$0.30
D1	Continental Device India Limited	1N4148	Jaycar	ZR1100	5	\$0.95
D2	Continental Device India Limited	1N4148	Jaycar	ZR1100	5	\$0.95
J1	Generic	Battery holder, 3V, 2xAA, flying leads	Jaycar	PH9202	1	\$1.45
R1	Generic	Resistor, Axial, Metal Film, 27k 1% 0.5W	Jaycar	RR0606	8	\$0.85
R2	Generic	Resistor, Axial, Carbon Film, 10k 5% 1W	Jaycar	RR2798	2	\$0.68
R3	Generic	Resistor, Axial, Carbon Film, 10k 5% 1W	Jaycar	RR2798	2	\$0.68
S1	NKK Switches	SS12SDP4	Digikey	360-2922-ND	1	\$4.22
U1	Texas Instruments	SN74HC14N	Jaycar	ZC4821	1	\$1.45
U1	Generic	IC socket, DIP-14	Jaycar	PI-6501	1	\$0.40
X1	TDK	PS1720P02	Element14	1669968	1	\$1

Table 1 – Bill of materials (BoM) for PCB siren design.

5. Assembly overlay

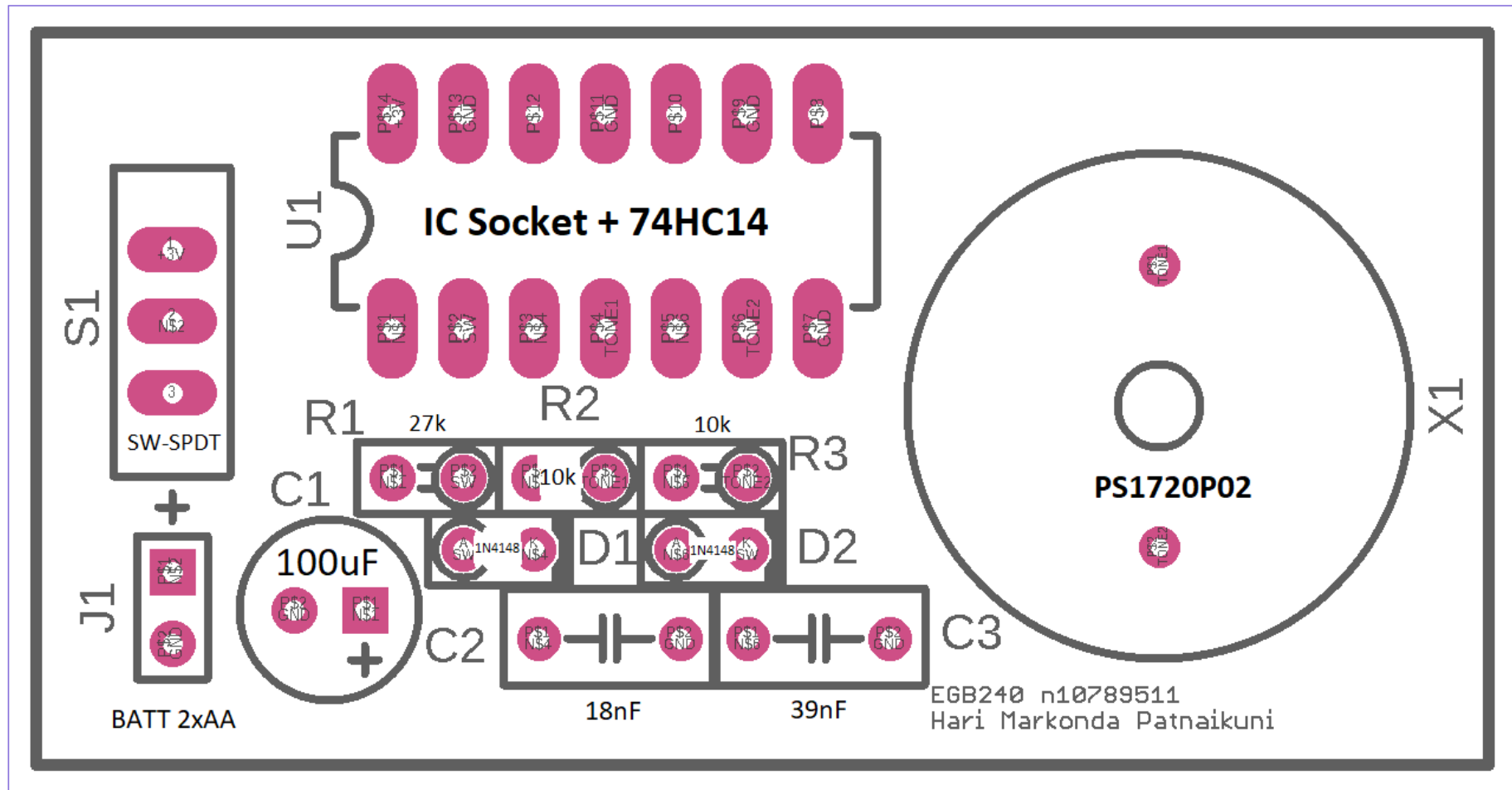

Note: Solder IC Socket in U1 position prior to inserting IC.

Figure 5 – Assembly overlay and instructions for siren circuit PCB design.

6. Photos of assembled prototype

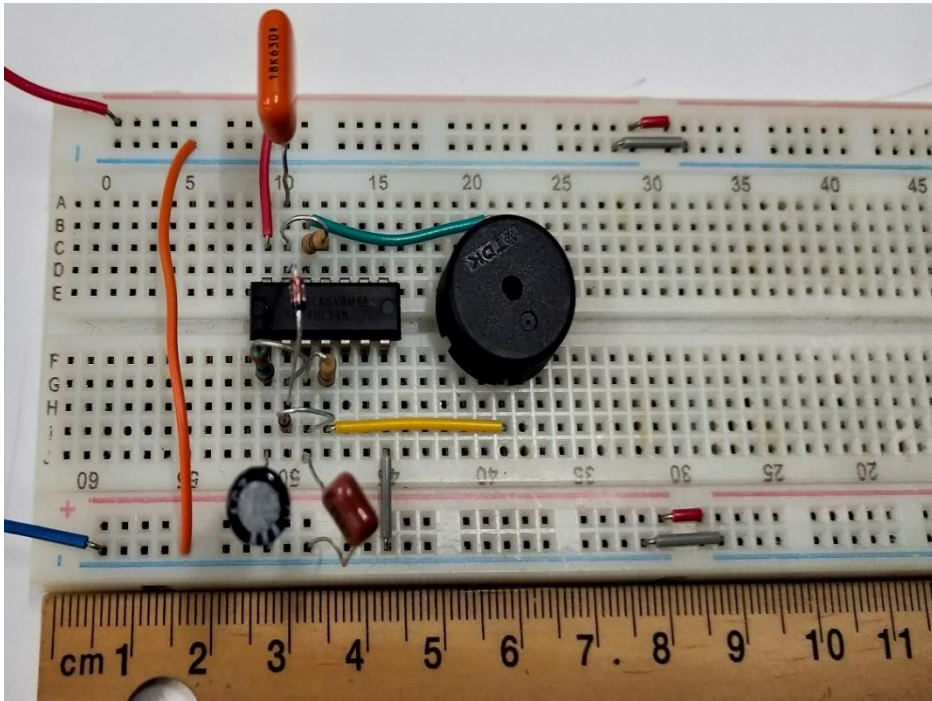


Figure 6 – Constructed prototype on breadboard showing power supply connections (Red – 3V, Blue 0V) and scale in centimetres.

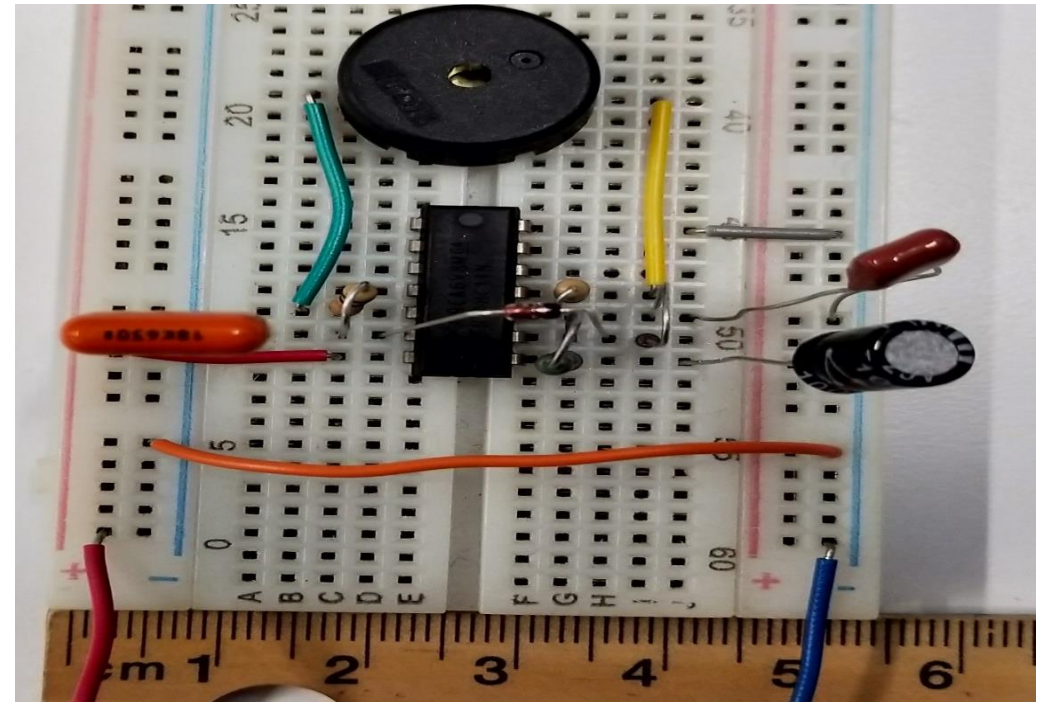


Figure 7 – Alternate view of prototype on breadboard. Scale in centimetres.

7. Simulation circuit and results

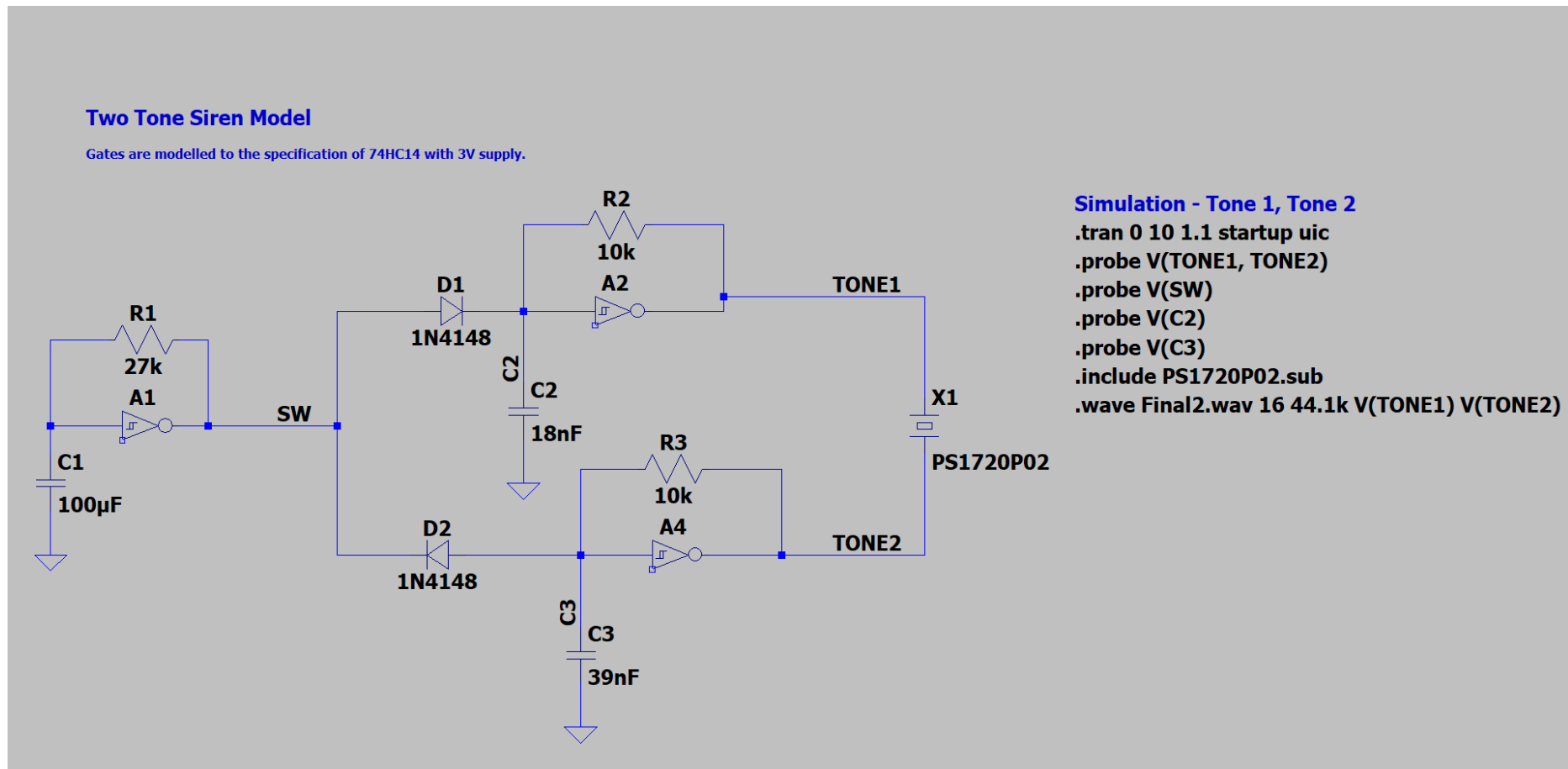


Figure 8 – LTspice Schematic with simulation command. Schematic details included in netlist of Figure – 9. All simulation results found in Figures 10 to 15 correspond to Simulation – Tone 1, Tone 2.

Simulation model netlist (LTspice)

* Two Tone Siren Model

* Simulation - Tone 1, Tone 2

```
.tran 0 10 1.1 startup uic
.wave Final2.wav 16 44.1k V(TONE1) V(TONE2)
.probe V(TONE1, TONE2)
.probe V(SW)
.probe V(C2)
.probe V(C3)
```

* Gates are modelled to the specification of 74HC14 with 3V supply.

```
A2 C2 0 0 0 0 TONE1 0 0 SCHMITT Vhigh=3 Rhigh=34 Rlow=41 Cout=200p Vt=1.27 Vh=0.40 td=31n
R2 TONE1 C2 10k
C2 C2 0 18nF
XX1 TONE1 TONE2 PS1720P02
A1 N001 0 0 0 0 SW 0 0 SCHMITT Vhigh=3 Rhigh=34 Rlow=41 Cout=200p Vt=1.27 Vh=0.40 td=31n
R1 SW N001 27k
C1 N001 0 100µF
D1 SW C2 1N4148
A4 C3 0 0 0 0 TONE2 0 0 SCHMITT Vhigh=3 Rhigh=34 Rlow=41 Cout=200p Vt=1.27 Vh=0.40 td=31n
R3 TONE2 C3 10k
C3 C3 0 39nF
D2 C3 SW 1N4148
```

```
.lib C:\Users\hmark\Documents\LTspiceXVII\lib\cmp\standard.dio
```

```
.include PS1720P02.sub
```

```
.backanno
.end
```

Figure 9 – Netlist for LTspice Schematic found in Figure 8.

Simulation model SW plot (LTspice)

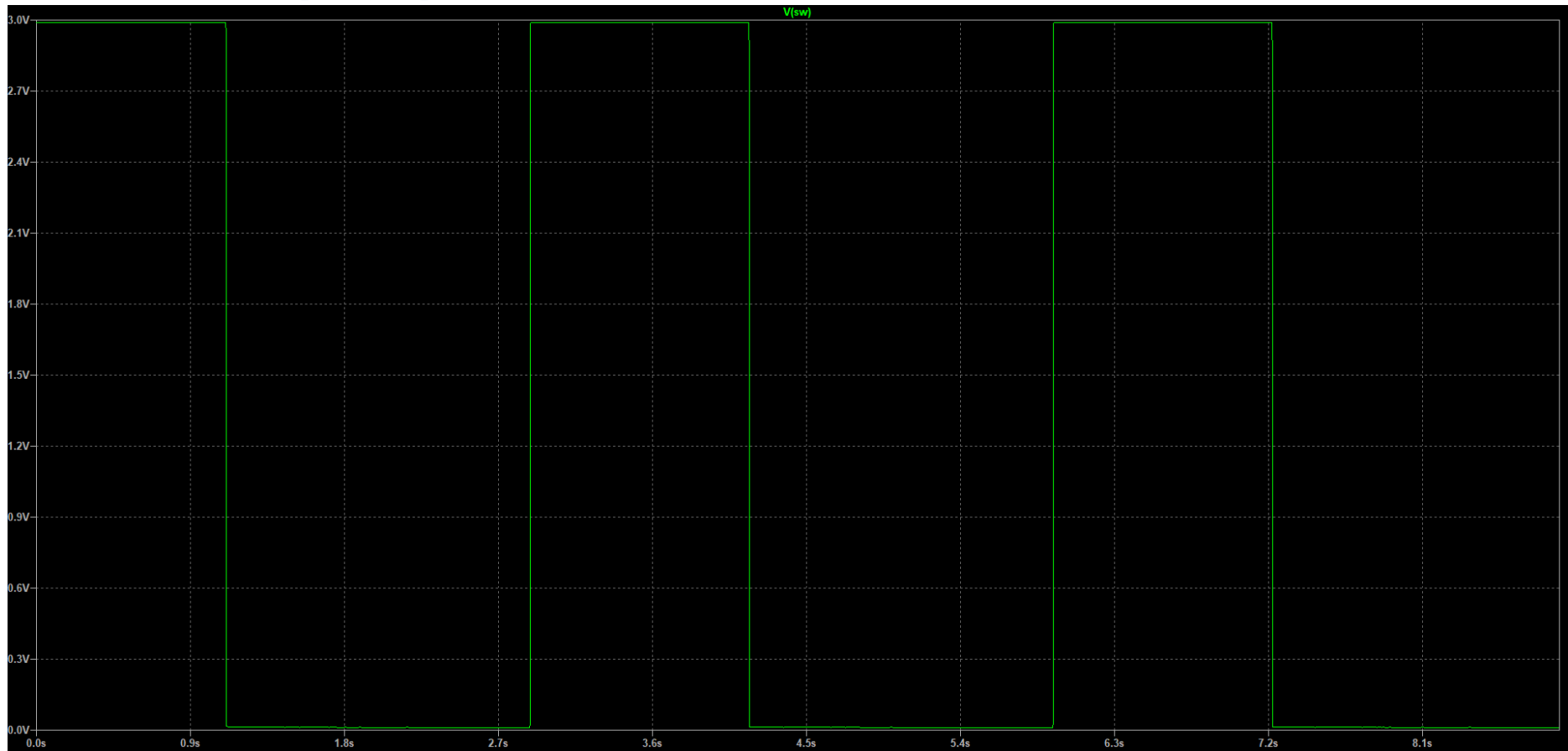


Figure 10 – LTspice plot of SW node shown in Figure 8. Shows frequency of oscillation at 0.296 Hz.

Simulation model TONE1 plot (LTspice)

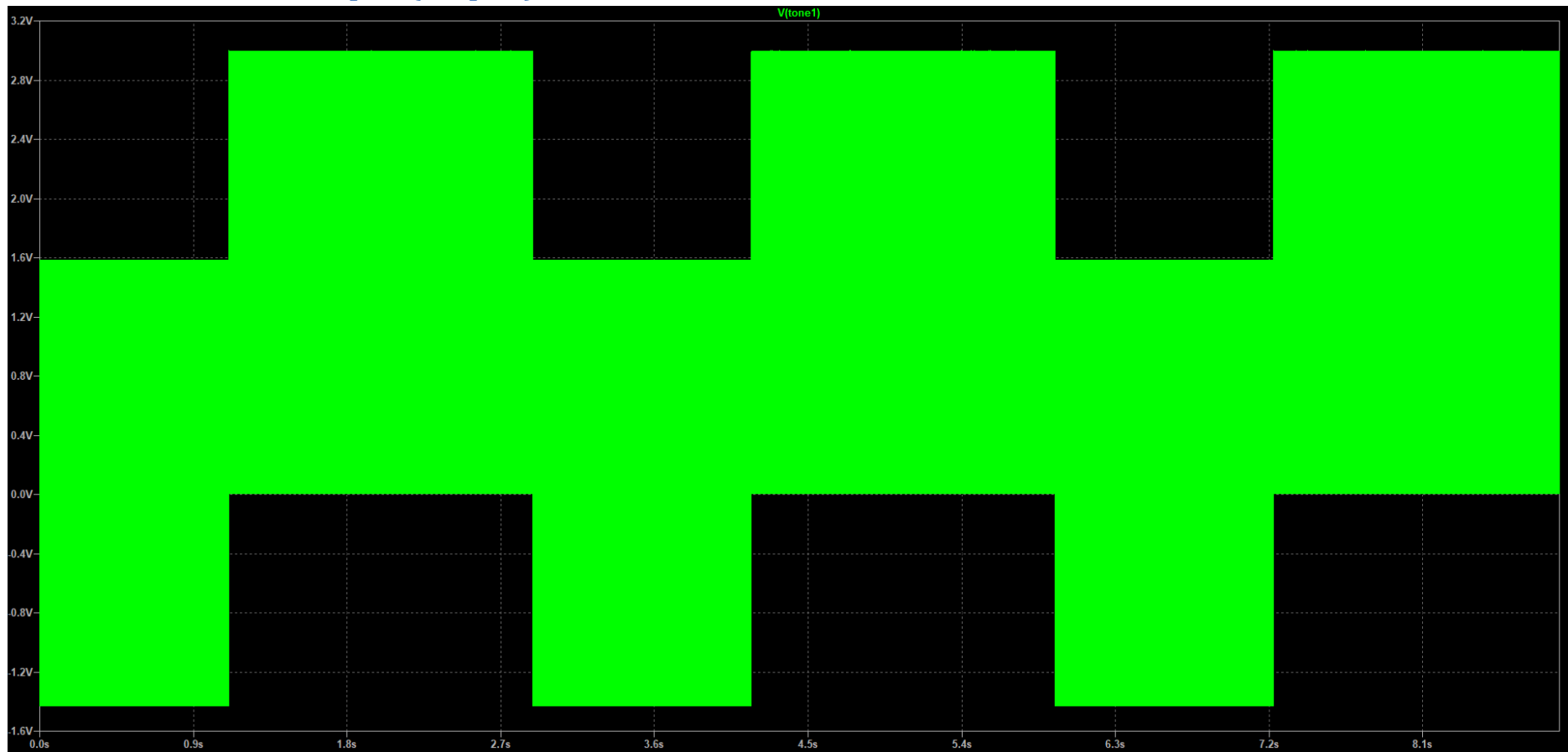


Figure 11 - LTspice plot of TONE1 node of buzzer shown in Figure 8. Shows frequency of TONE1 at 4.44 kHz.

Simulation model TONE2 plot (LTspice)

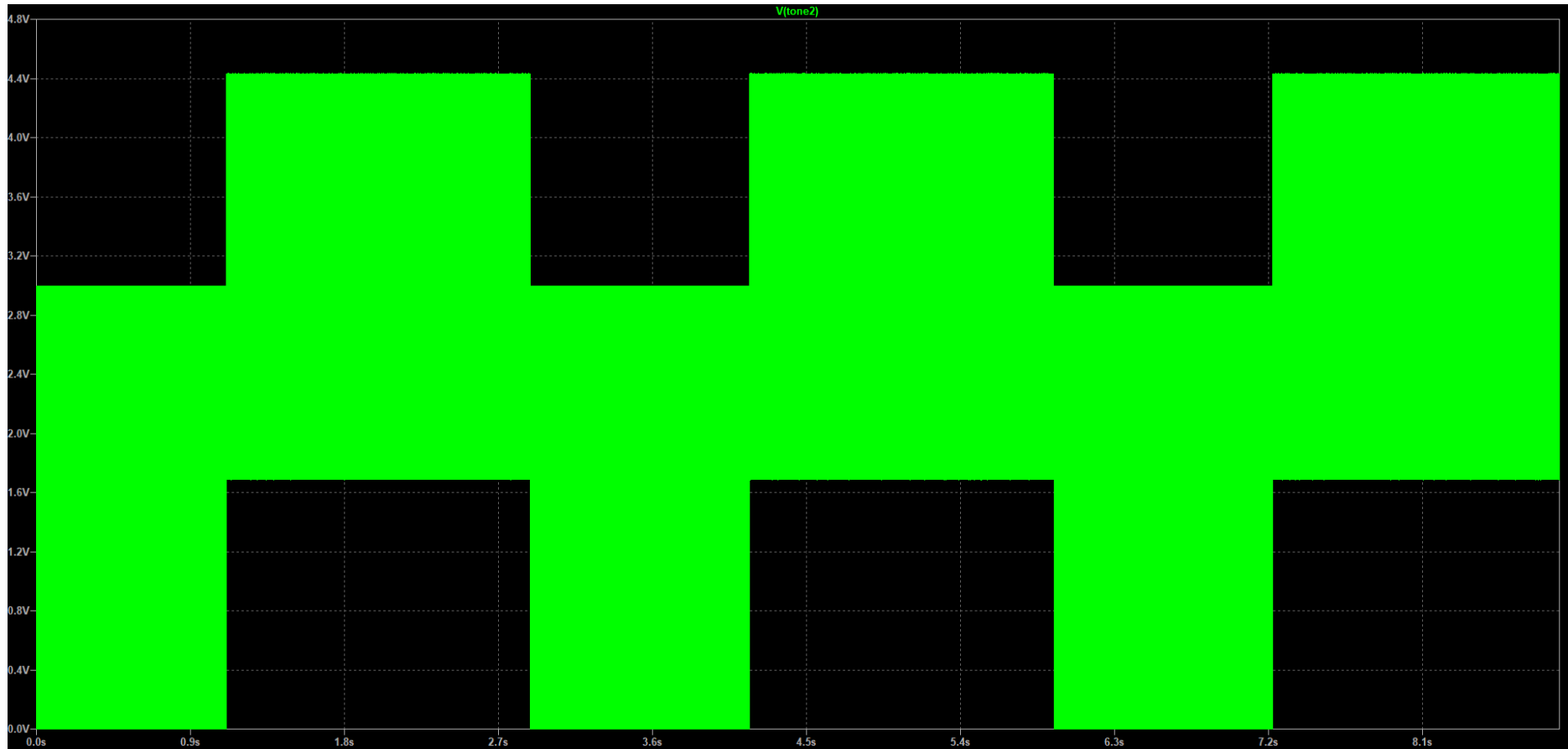


Figure 12 - LTspice plot of TONE2 node of buzzer shown in Figure 8. Shows frequency of TONE2 at 2.051 kHz.

Simulation model TONE1 and TONE2 plot (LTspice)

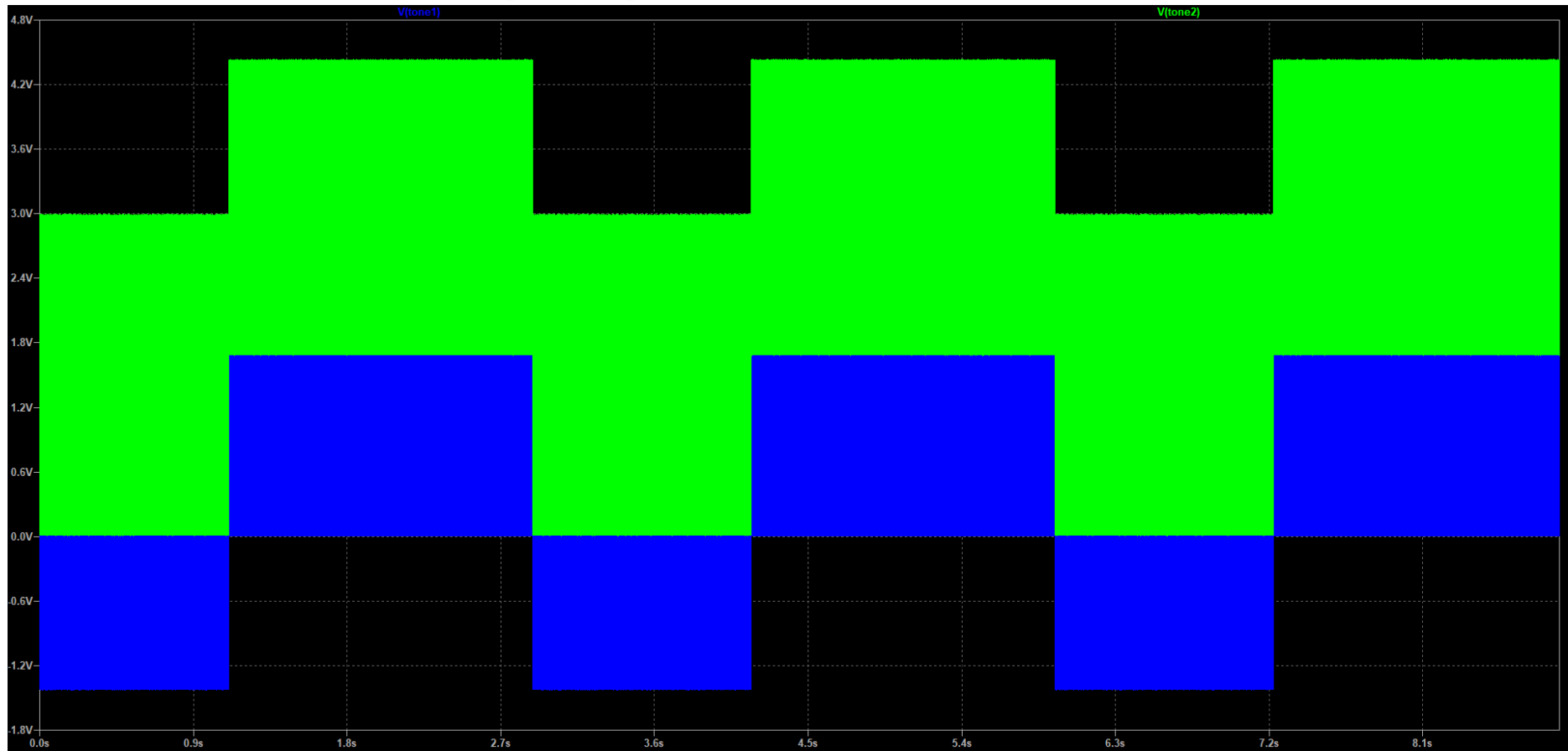


Figure 13 - LTspice plot of TONE 1 and 2 nodes of buzzer shown in Figure 8.

Simulation model C2 charge and discharge plot (LTspice)

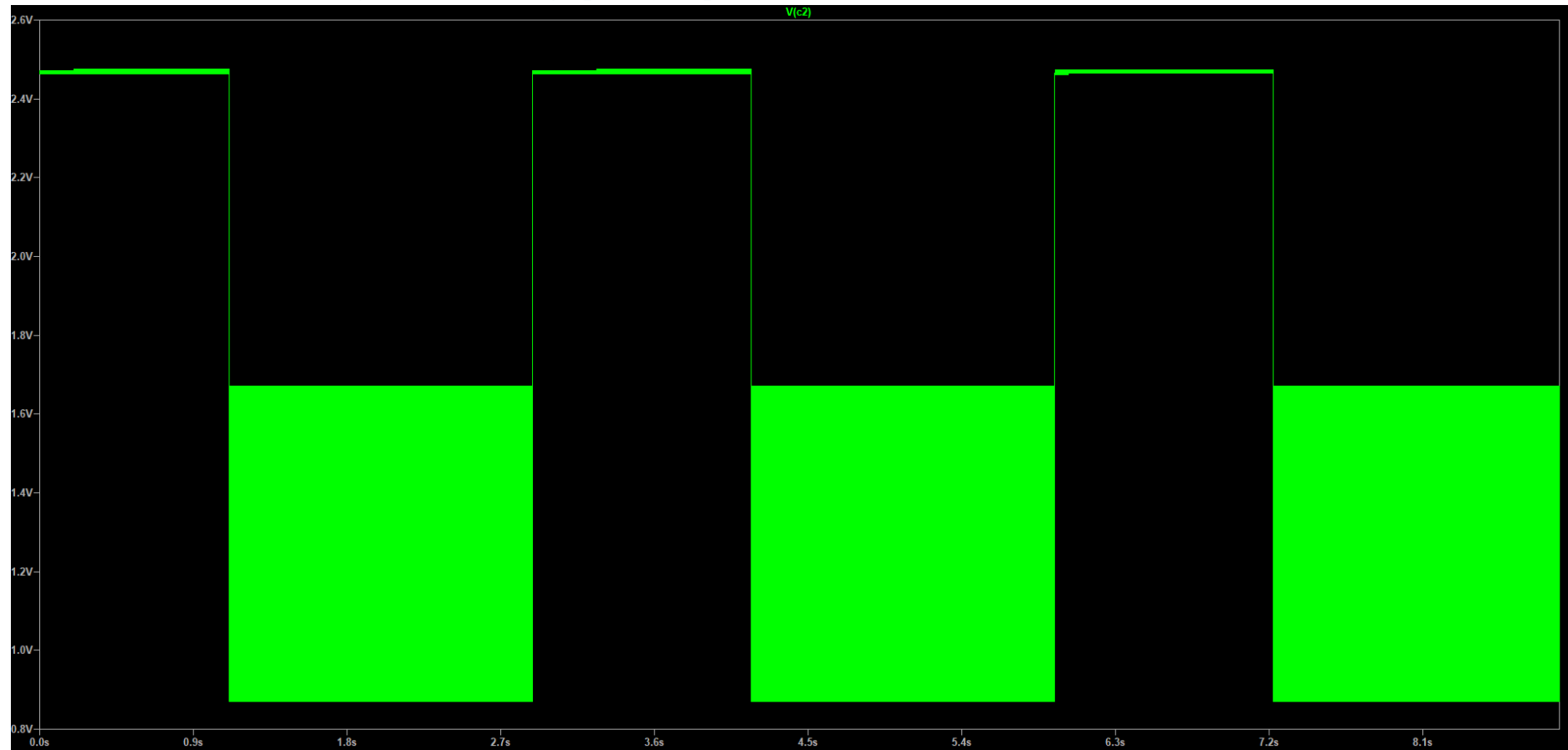


Figure 14 - LTspice plot of C2 node shown in Figure 8.

Simulation model C3 charge and discharge plot (LTspice)

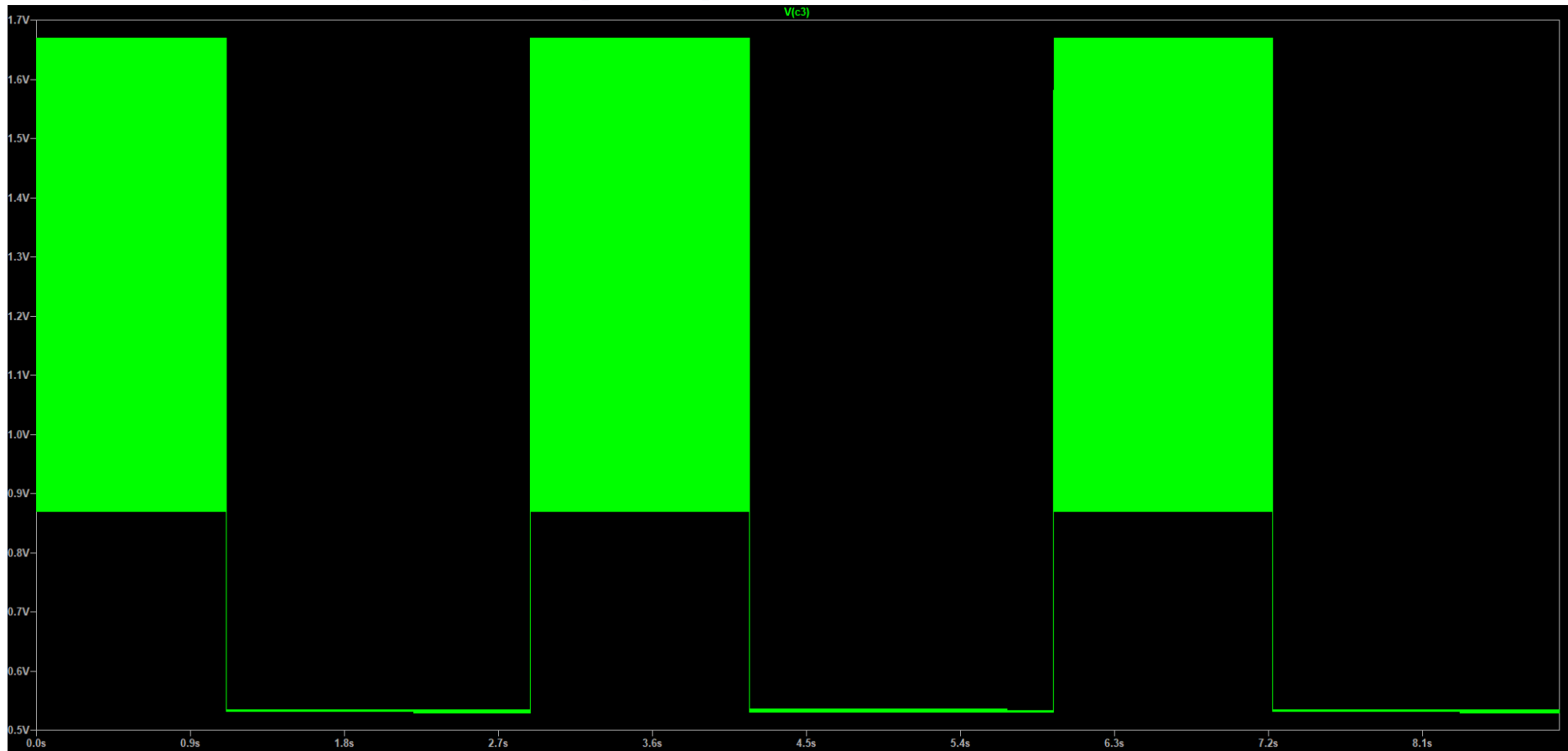


Figure 15 - LTspice plot of C3 node shown in Figure 8.

8. Experimental results

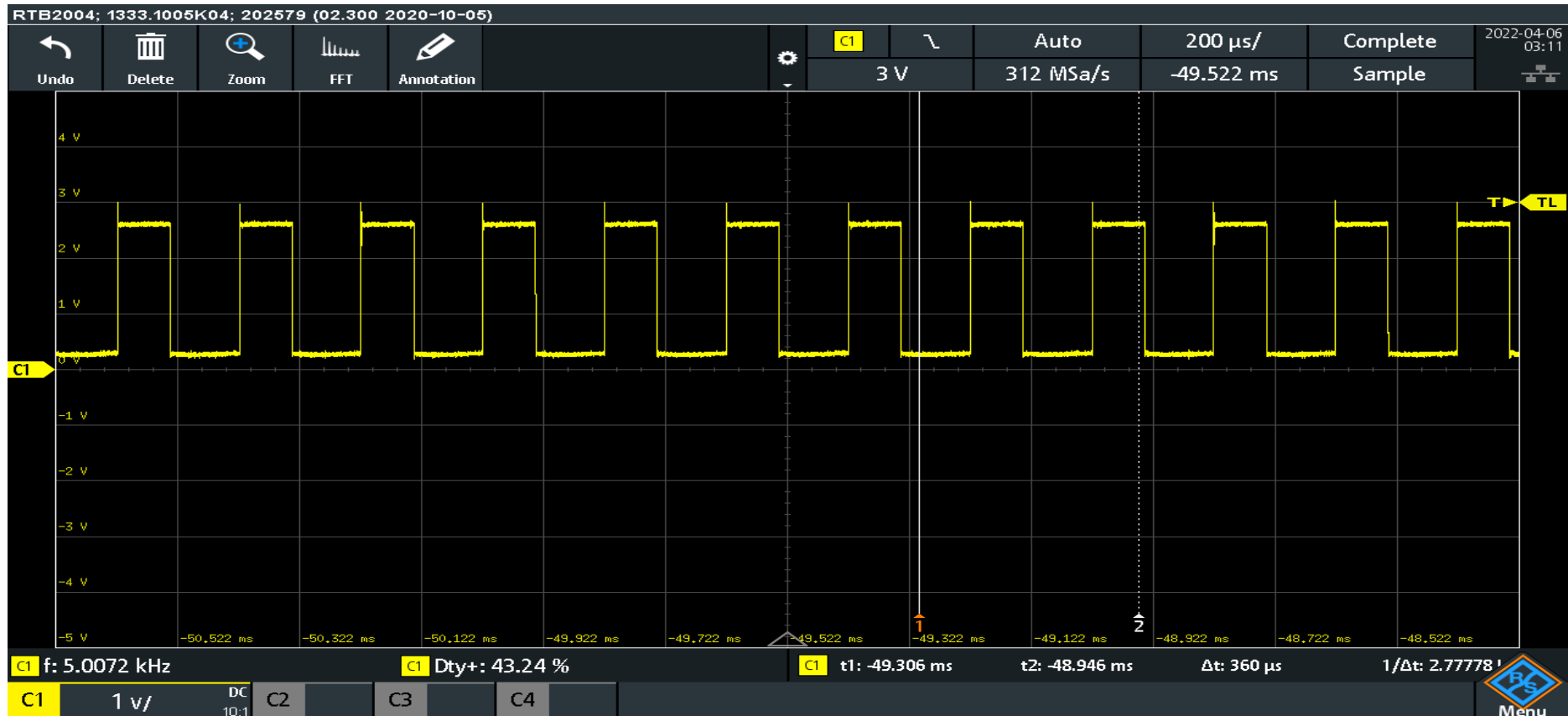


Figure 16 –TONE1(C1, yellow, 0.5V/div) waveform showing frequency of 5 kHz($\approx 11\%$ higher than theoretical frequency(4.44 kHz)) and duty cycle of 43.2%

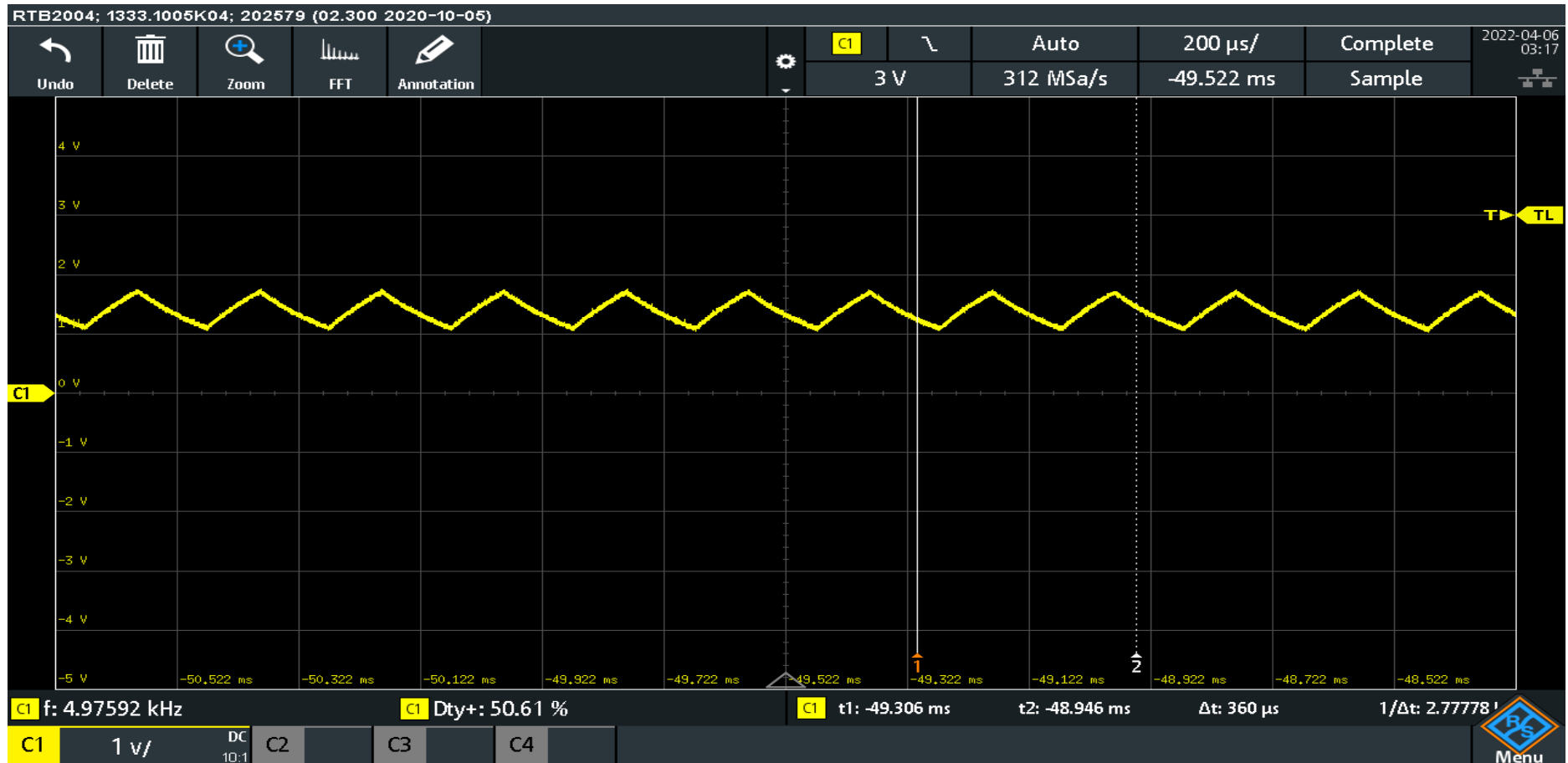


Figure 17 – C1(yellow, 0.5V/div) C2(18nF) charge and discharge waveform

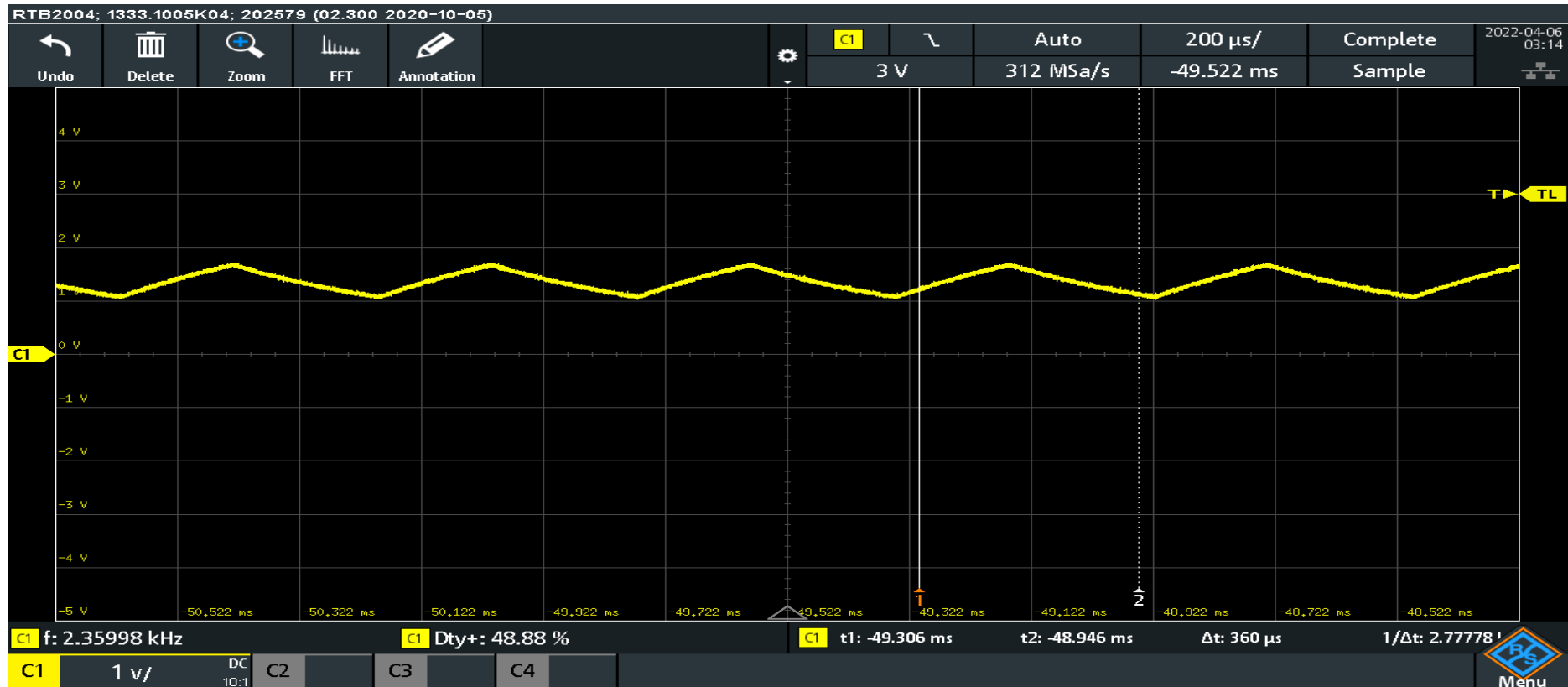


Figure 18 – C1(yellow, 0.5V/div) C3(39nF) charge and discharge waveform

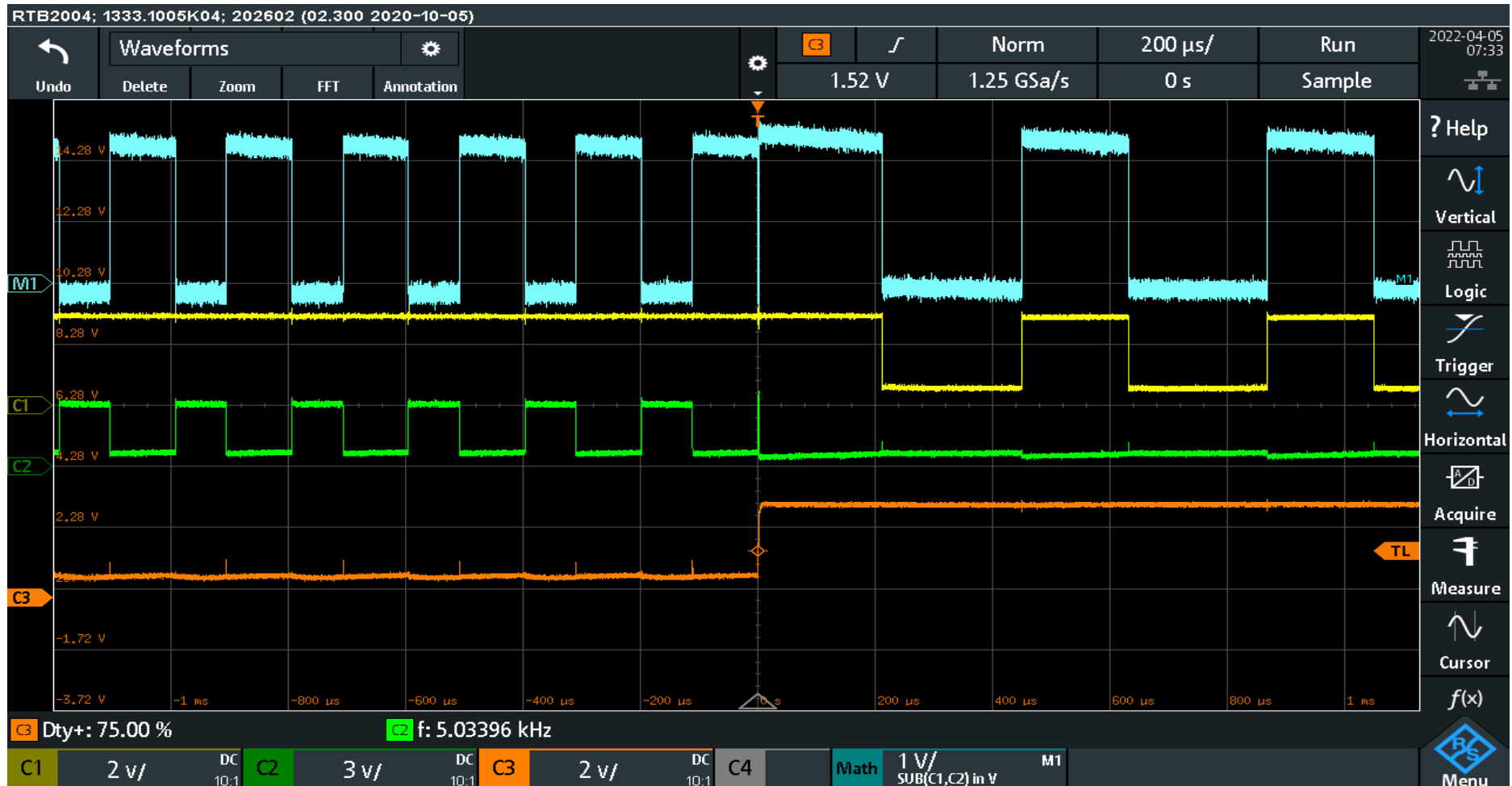


Figure 19 – M1(turquoise, 0.5V/div) shows math function depicting tone alternating, C1(yellow, 0.5V/div) shows tone 2, C2(green, 0.5V/div) shows tone 1, C3(orange, 0.5V/div) shows trigger oscillator at 0.296 Hz switching between low and high.

References

NXP. (2012, 9 19). *74HC14; 74HCT14 Hex inverting Schmitt trigger*. Retrieved 4 7, 2022, from Octopart: <https://datasheet.octopart.com/74HC14N%2C652-NXP-Semiconductors-datasheet-141446461.pdf>

TDK. (2022, 2). *piezoelectronic_buzzer_ps_en.pdf*. Retrieved 4 7, 2022, from TDK: https://product.tdk.com/system/files/dam/doc/product/sw_piezo/sw_piezo/piezo-buzzer/catalog/piezoelectronic_buzzer_ps_en.pdf